

CECS 225

Lab 3

Ronnie Casasola

012737398

Section 1: ALU_Decoder Verilog module source

```
`timescale 1ns / 1ps
```

```
module ALU_Decoder( ALUOp, Funct, ALUControl );
```

```
    input [1:0] ALUOp;
```

```
    input [5:0] Funct;
```

```
    output [2:0] ALUControl;
```

```
        assign ALUControl[2] = ALUOp[0] | (ALUOp[1] & Funct[1]);
```

```
        assign ALUControl[1] = !ALUOp[1] | (ALUOp[1] & !Funct[2]);
```

```
        assign ALUControl[0] = ALUOp[1] & Funct[3] & Funct[0];
```

```
endmodule
```

Section 2: ALU_Decoder Verilog Test Fixture

```
`timescale 1ns / 1ps
```

```
module ALU_Decoder_Tester;
```

```
    // Inputs
```

```
    reg [1:0] ALUOp;
```

```
    reg [5:0] Funct;
```

```
    // Outputs
```

```
    wire [2:0] ALUControl;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    ALU_Decoder uut (
```

```
        .ALUOp(ALUOp),
```

```
        .Funct(Funct),
```

```
        .ALUControl(ALUControl)
```

```
    );
```

```
    initial begin
```

```
        //Test Case 0
```

```
        ALUOp = 2'b0;
```

```
        Funct = 6'bx;
```

```
#10;
```

```
//Test Case 1
```

```
ALUOp = 2'b01;
```

```
Funct = 6'bx;
```

```
#10;
```

```
//Test Case 2
```

```
ALUOp = 2'b10;
```

```
Funct = 6'bx0000;
```

```
#10;
```

```
//Test Case 3
```

```
ALUOp = 2'b10;
```

```
Funct = 6'bx0010;
```

```
#10;
```

```
//Test Case 4
```

```
ALUOp = 2'b10;
```

```
Funct = 6'bx0100;
```

```
#10;
```

```
//Test Case 5
```

```
ALUOp = 2'b10;
```

```
Funct = 6'bx0101;
```

```
#10;
```

```
//Test Case 6
```

```
ALUOp = 2'b10;
```

```
Funct = 6'bxx1010;
```


```
#10;
```

```
$stop;
```

```
end
```

```
endmodule
```

Section 3: ALU_Decoder Simulation Wavelength screenshot

 

Section 4: Main_Decoder Verilog module source

```
`timescale 1ns / 1ps
```

```
module Main_Decoder(
```

```
    input [5:0] Opcode,
```

```
    output [1:0] ALUOp,
```

```
    output RegWrite,
```

```
    output RegDst,
```

```
    output ALUSrc,
```

```
    output Branch,
```

```
    output MemWrite,
```

```
    output MemtoReg
```

```
);
```

```
    wire R_Format, lw, sw, beq;
```

```
    assign R_Format =  
~Opcode[5]*~Opcode[4]*~Opcode[3]*~Opcode[2]*~Opcode[1]*~Opcode[0];
```

```
    assign lw = Opcode[5]*~Opcode[4]*~Opcode[3]*~Opcode[2]*Opcode[1]*Opcode[0];
```

```
    assign sw = Opcode[5]*~Opcode[4]*Opcode[3]*~Opcode[2]*Opcode[1]*Opcode[0];
```

```
    assign beq =  
~Opcode[5]*~Opcode[4]*~Opcode[3]*Opcode[2]*~Opcode[1]*~Opcode[0];
```

```
    assign RegWrite =  
(~Opcode[4]*~Opcode[3]*~Opcode[2])*(Opcode[5]+~Opcode[1])*(~Opcode[5]+Opcode[0])*(  
Opcode[0]+~Opcode[1])*(Opcode[1]+Opcode[0]);
```

```
    assign RegDst = ~(Opcode[5] + Opcode[4] + Opcode[3] + Opcode[2] + Opcode[1] +  
Opcode[0]);
```

```
    assign ALUSrc = (Opcode[5] * ~Opcode[4] * ~Opcode[2] * Opcode[1] * Opcode[0]);
```

```
    assign Branch =  
~Opcode[5]*~Opcode[4]*~Opcode[3]*Opcode[2]*~Opcode[1]*~Opcode[0];  
  
    assign MemWrite =  
Opcode[5]*~Opcode[4]*Opcode[3]*~Opcode[2]*Opcode[1]*Opcode[0];  
  
    assign MemtoReg =  
Opcode[5]*~Opcode[4]*~Opcode[3]*~Opcode[2]*Opcode[1]*Opcode[0];  
  
    assign ALUOp[1] =  
~Opcode[5]*~Opcode[4]*~Opcode[3]*~Opcode[2]*~Opcode[1]*~Opcode[0];  
  
    assign ALUOp[0] =  
~Opcode[5]*~Opcode[4]*~Opcode[3]*Opcode[2]*~Opcode[1]*~Opcode[0];  
  
endmodule
```


Section 5: Main_Decoder Verilog Test fixture

`timescale 1ns / 1ps

```
module Main_Decoder_Tester;
```

```
    // Inputs
```

```
    reg [5:0] Opcode;
```

```
    // Outputs
```

```
    wire [1:0] ALUOp;
```

```
    wire RegWrite;
```

```
    wire RegDst;
```

```
    wire ALUSrc;
```

```
    wire Branch;
```

```
    wire MemWrite;
```

```
    wire MemtoReg;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    Main_Decoder uut (
```

```
        .Opcode(Opcode),
```

```
        .ALUOp(ALUOp),
```

```
        .RegWrite(RegWrite),
```

```
        .RegDst(RegDst),
```

```
        .ALUSrc(ALUSrc),
```

```
        .Branch(Branch),
```

```
        .MemWrite(MemWrite),
```

```
        .MemtoReg(MemtoReg)
```

```
    );
```

```
initial begin

    //Test case 0
    Opcode = 6'b000000;
    #10;

    //Test case 1
    Opcode = 6'b100011;
    #10;

    //Test case 2
    Opcode = 6'b101011;
    #10;


    //Test case 3
    Opcode = 6'b000100;
    #10;

    //Test case 4
    Opcode = 6'b111111;
    #10;
    $stop;

end

endmodule
```

Section 6: Main_Decoder simulation waveform screenshot

 

Section 7: Control_Unit Verilog module source

```
`timescale 1ns / 1ps
```

```
module Control_Unit(  
    input [5:0] Opcode,  
    input [5:0] Funct,  
    output MemtoReg,  
    output MemWrite,  
    output Branch,  
    output ALUSrc,  
    output RegDst,  
    output RegWrite,  
    output [2:0] ALUControl  
);
```

```
    wire [1:0] ALUOp_md_to_ad;
```

```
    ALU_Decoder ad(  
        .ALUOp(      ),  
        .Funct(      ),  
        .ALUControl(  )  
    );
```

```
    Main_Decoder md(  
        .Opcode(      ),  
        .RegWrite(    ),  
        .RegDst(      ),
```

```
.ALUSrc(      ),  
.Branch(      ),  
.MemWrite(    ),  
.MemtoReg(    ),  
.ALUOp(       )  
);
```

```
Endmodule
```

Section 8: Control_Unit Verilog Test Fixture

```
`timescale 1ns / 1ps
```

```
module Control_Unit_Tester;
```

```
    // Inputs
```

```
    reg [5:0] Opcode;
```

```
    reg [5:0] Funct;
```

```
    // Outputs
```

```
    wire MemtoReg;
```

```
    wire MemWrite;
```

```
    wire Branch;
```

```
    wire ALUSrc;
```

```
    wire RegDst;
```

```
    wire RegWrite;
```

```
    wire [2:0] ALUControl;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    Control_Unit uut (
```

```
        .Opcode(Opcode),
```

```
        .Funct(Funct),
```

```
        .MemtoReg(MemtoReg),
```

```
        .MemWrite(MemWrite),
```

```
        .Branch(Branch),
```

```
        .ALUSrc(ALUSrc),
```

```
.RegDst(RegDst),  
.RegWrite(RegWrite),  
.ALUControl(ALUControl)  
);
```

```
initial begin
```

```
//Test case 0
```

```
Opcode = 6'b0000000;
```

```
Funct = 6'b100000;
```

```
#10;
```

```
//Test case 1
```

```
Opcode = 6'b0000000;
```

```
Funct = 6'b100010;
```

```
#10;
```

```
//Test case 2
```

```
Opcode = 6'b0000000;
```

```
Funct = 6'b100100;
```

```
#10;
```

```
//Test case 3
```

```
Opcode = 6'b0000000;
```

```
Funct = 6'b100101;
```

```
#10;
```

```
//Test case 4
```

```
Opcode = 6'b0000000;  
Funct = 6'b101010;  
#10;
```

```
//Test case 5  
Opcode = 6'b100011;  
Funct = 6'bx;  
#10;
```

```
//Test case 6  
Opcode = 6'b101011;  
Funct = 6'bx;  
#10;
```

```
//Test case 7  
Opcode = 6'b000100;  
Funct = 6'bx;  
#10;
```

```
//Test case 8  
Opcode = 6'b111111;  
Funct = 6'bx;  
#10;
```

```
$stop;
```

```
end
```

```
endmodule
```


Section 9: Control_Unit simulation screenshot

